
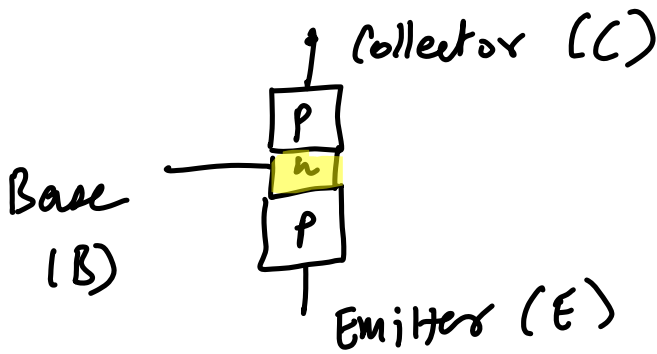





Bipolar Junction Transistors

npn transistor
pnp transistor

Schematic

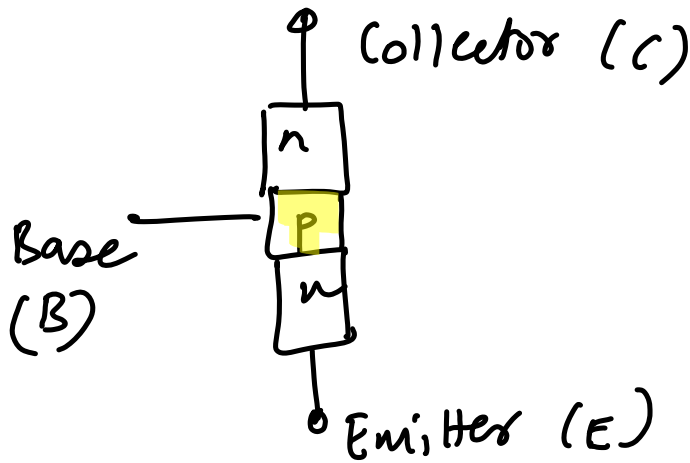


Symbols

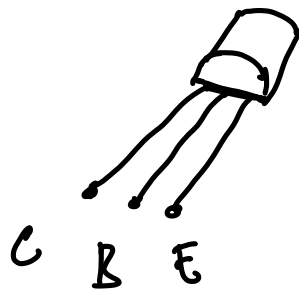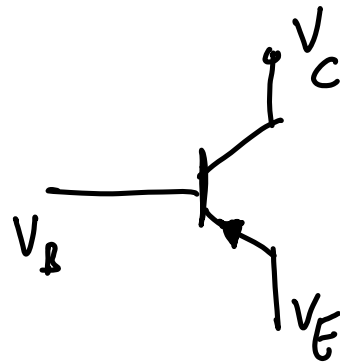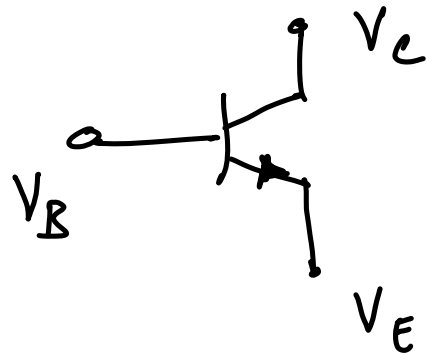

2N 3904



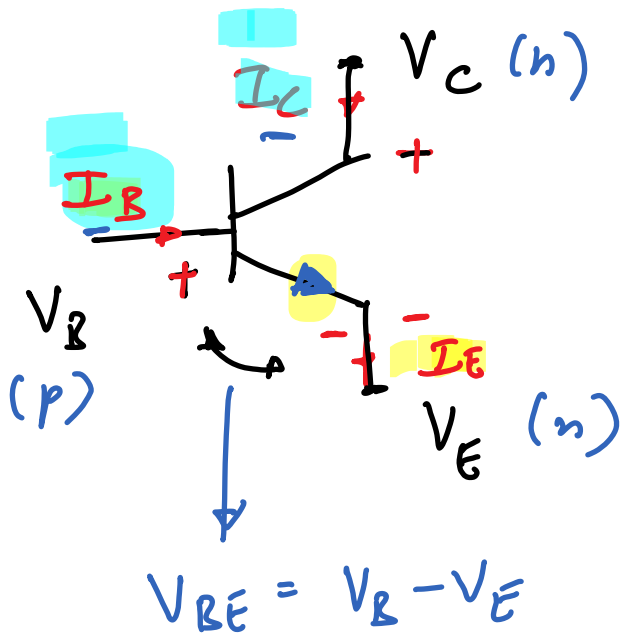Emitter is more heavily doped than the collector





- BE is forward biased
- BC is reverse biased
- Electrons flow from E to B OR Current flows from B to E
- $I_E = I_C + I_B$
- $I_C = \beta I_B$ (Active mode)
 $\beta \approx 100$ \downarrow small I_B leads to a big I_C

BJT working

3 modes

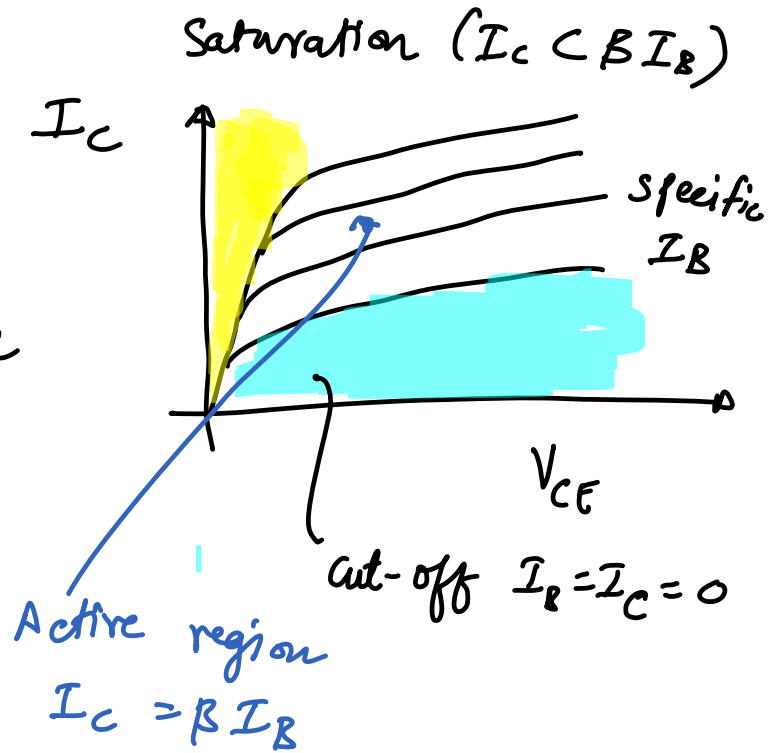- ① Cut-off mode
- ② Saturation mode
- ③ Active mode



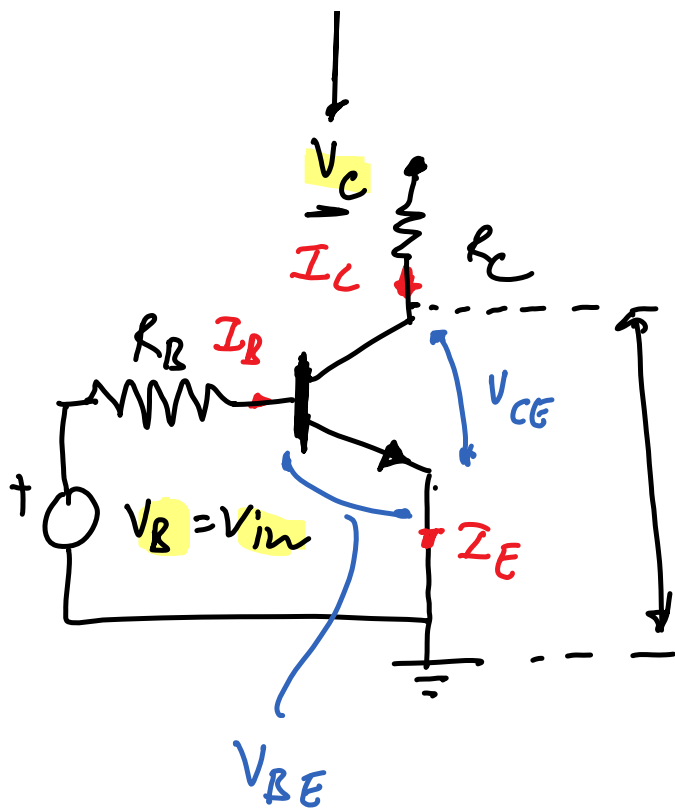

① Cut-off


$$I_B = I_C = 0$$

$$V_{BE} < 0.7$$

V_{out}

$$V_{out} = V_C$$

connected to LED

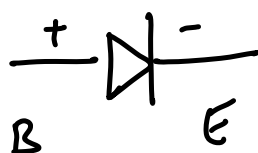

$$V_{BE} = 0.7$$

② Saturation

$$I_B > 0 \quad I_C > 0$$

$$V_{BE} \geq 0.7 \text{ V}$$

$$V_{out} = V_{CE} = 0.2 \approx 0$$

BJT as a switch by
 cycling between cut-off &
 Saturation

③ Active mode

$$I_B > 0 ; I_C > 0 ;$$

$$\Rightarrow V_{BE} \geq 0.7 \text{ V}$$

$$0.2 \leq V_{out} = V_{CE} \leq V_C$$

$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

always true

By changing $V_B = V_{in}$ we are able to vary V_{out} from 0.2 to V_C

BJT is a linear amplifier in the active mode